


Why do we use imaginary numbers  
in AC circuit analysis with capacitors  
and Inductors?

Author: Ahmed Khedr Elsheshtawy

Signature: Ahmed  
Elsheshtawy.

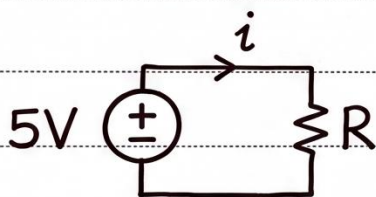
## Why do we use imaginary numbers in AC Circuit analysis?

In DC, when having only a resistor: ratio between  $V$  and  $I$  stays the same at any time  $t$  ( $R = V/I$ ), hence  $V$  and  $I$  are in phase. Same thing occurs in AC when we have only a resistor.




$$i = \frac{V}{R}$$

$$\phi = 0$$

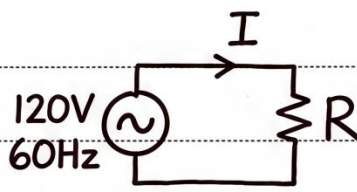

$$I = \frac{V}{R}$$

$$\phi = 0$$

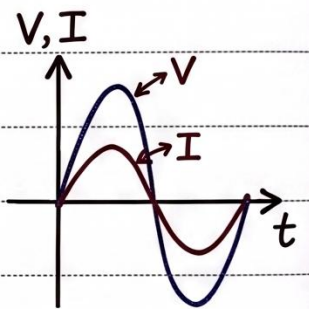

...With capacitors or inductors, this isn't the case...

$$i = C \frac{dv}{dt}$$

$$v = L \frac{di}{dt}$$

Clearly not in phase  
when using sinusoidal

$$v = \sin t$$

functions (sin, cos)

$$C = 1 \Rightarrow i = \cos t = \sin(t + 90^\circ)$$

Now, we can apply KCL here, but that would be messy.

Applying KVL:


$$V_S = V_R + V_L + V_C$$

$$V_S = V_{rms} \cos(t)$$

$$V_R = V_{Rmax} \cos(t)$$

$$V_L = V_{Lmax} \cos(t + 90^\circ)$$

$$V_C = V_{Cmax} \cos(t - 90^\circ)$$

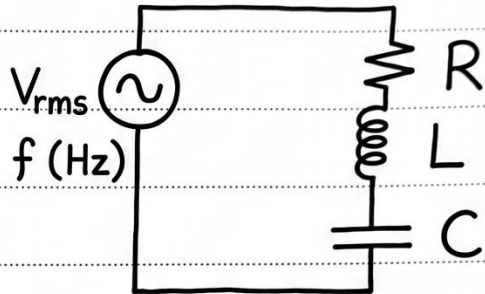

$$V_{rms} \cos(t) = V_{Rmax} \cos(t) + V_{Cmax} \cos(t - 90^\circ) + V_{Lmax} \cos(t + 90^\circ)$$

→ For a simple circuit, this equation is too difficult to deal with. You can use sine and cosine rules

$$\sin(\alpha \pm \beta) = \sin\alpha \cos\beta \pm \sin\beta \cos\alpha$$

$$\cos(\alpha \pm \beta) = \cos\alpha \cos\beta \mp \sin\alpha \sin\beta$$

Now to find any unknown (like  $V_{Rmax}$ ), you would require using trig identities and experience math trauma.

OR, you can use Euler's formula:

$$e^{i\theta} = \cos(\theta) + i \sin(\theta)$$

→ any trig expression can be rewritten as exponential.

$$\text{Also! see: } 1 + i = \sqrt{2} \cos(45^\circ) + i(\sqrt{2} \sin(45^\circ)) = \sqrt{2} e^{i(45^\circ)}$$

there is always a way to write complex number in this format.

~~For a capacitor. If we say  $V = I / 2\pi C$ , but if we ignore phase for a moment and assume the equation:~~

Where the hell did this come from?

let's say Voltage across a component is  $V_{\text{comp}} = A \cos(t + \phi_{\text{comp}})$ , and we want to find the current across it. We can't just multiply  $V_{\text{comp}}$  by a constant to get the equation of  $I_{\text{comp}}$  sure multiplying by  $(-1)$  can phase shift by  $180^\circ$ , but we don't even know if  $I$  is shifted by  $180^\circ$ . So what do we do?

let's <sup>observe</sup> ~~see~~ this beauty for a second to see if it can benefit us:

$$e^{i\theta} = \cos \theta + i \sin \theta$$

$$2e^{i30^\circ} = 2 \cos(30^\circ) + 2i \sin(30^\circ)$$

multiply both:

$$e^{i\theta} \times 2e^{i30^\circ} = 2e^{i\theta+i30^\circ} = 2e^{i(\theta+30^\circ)}$$

$$2e^{i(\theta+30^\circ)} = 2 \cos(\theta+30^\circ) + 2i \sin(\theta+30^\circ)$$

by multiplying two functions, we got a new function that has a magnitude of  $2$  and phase shifted  $30^\circ$ .

Surely we can use this in our main problem of  $V_{\text{comp}}$  and  $I_{\text{comp}}$  to find  $I_{\text{comp}}$  across a capacitor or an inductor.

You can also use Euler's formula to find the math identity of any sinusoid function.

For example:

$$\cos(2\theta) = ?$$

we can just place that as the angle in Euler's formula

$$\Rightarrow e^{2\theta i} = \cos(2\theta) + i \sin(2\theta)$$

Hey! this is the same function we wanted to find its value!

How can we find it? we can evaluate  $e^{2\theta i} \neq$  and find its real component, and that real component would equal  $\cos(2\theta)$

$$\begin{aligned} e^{2\theta} &= e^{2(i\theta)} = (e^{i\theta})^2 = (\cos \theta + i \sin \theta)^2 \\ &= \cos^2 \theta + 2i \cos \theta \sin \theta - \sin^2 \theta \leftarrow i^2 = -1 \\ &= \underbrace{\cos^2 \theta - \sin^2 \theta}_{\text{real component}} + i \underbrace{2 \cos \theta \sin \theta}_{\text{imaginary component}} \end{aligned}$$

$$\text{So, } \cos 2\theta = \cos^2 \theta - \sin^2 \theta$$

Also, if we set imaginary components equal to one another:

$$i \sin 2\theta = i 2 \sin \theta \cos \theta$$

Now let's apply that to the capacitor equation:  $i = C \frac{du}{dt}$

note: to avoid confusion with current ( $i$ ), imaginary symbol will be  $j$ .  $j = \sqrt{-1}$

if  $U = A \cos(\omega t + \phi)$ , and  $C = 1$  (for simplicity)  
So,  $i = -\omega CA \sin(\omega t + \phi)$

let's instead say:

$$U = A e^{j(\omega t + \phi)}$$

makes no sense, but the real component is our voltage

$$= A \cos(\omega t + \phi) + j A \sin(\omega t + \phi)$$

So, by the end we will see what the real component is

$$i = \frac{du}{dt} = \frac{d}{dt} (A e^{j(\omega t + \phi)}) = j\omega C A e^{j(\omega t + \phi)}$$

So, we can say,  $i = j\omega C \cdot \bar{V}$ \*

$$i = j\omega C \times (A \cos(\omega t + \phi) + j A \sin(\omega t + \phi))$$

$$= -\omega CA \sin(\omega t + \phi) + j\omega CA \cos(\omega t + \phi)$$

real component

is still  $i$  as we got normally by deriving  $(\frac{du}{dt})$

but! It + gave us an equation of that is equivalent but doesn't involve differentiation.


$$i = j\omega C \bar{V} \iff i = C \frac{du}{dt}$$

Now we can rearrange  $i = j\omega CV$  to:

$$\frac{v}{i} = \frac{1}{j\omega C} = X_c \quad \text{which is just the impedance of the capacitor to current.}$$

Notice:  $R = \frac{U}{i}$ , and  $X_c = \frac{U}{I}$  and the  $j$  of the imaginary numbers accounts for a phase shift of  $90^\circ$  just like  $\cos$  and  $\sin$ .

Now let's put a real example:

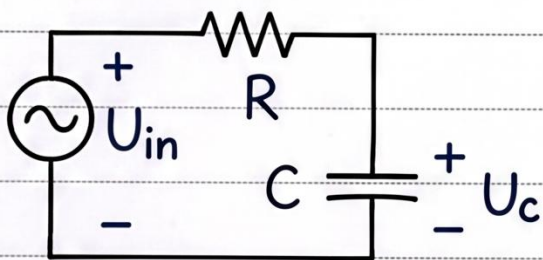

applying KVL:

$$U_{in} = U_c + U_R$$

$$U_R = iR = C \cdot \frac{dU_c}{dt} \cdot R = RC \cdot \frac{dU_c}{dt}$$

$$U_{in} = U_c + RC \cdot \frac{dU_c}{dt}$$

we know  $U_c$  would be of the form  $U_c = A \cos(\omega t + \theta)$ , but instead of substituting that, which wouldn't be fun, we can use the earlier function we came up with.

$$U_c = A e^{j(\omega t + \theta)}, \quad \text{and} \quad \frac{dU_c}{dt} = j\omega U_c$$

$$\text{So, } U_{in} = U_c + RC(j\omega U_c) = U_c(1 + j\omega RC)$$

and we finally get: 
$$U_c = \frac{1}{1 + j\omega RC} \cdot U_{in}$$

→  
cont.

For simplicity,  $\omega = C = R = 1$

$$V_c = \frac{1}{1+j} V_i = \frac{1}{1+j} \times \frac{1-j}{1-j} V_i$$

$$= \frac{1-j}{1-j^2} V_i = \frac{1-j}{1+1} V_i = \frac{1}{2} V_i - \frac{j}{2} V_i$$

$$V_c = \frac{1}{2} V_i - \frac{j}{2} V_i$$

so, if  $V_i = 3 \cos(t + 10^\circ)$

we can use euler's formula,  $V_i = 3e^{j(t+10^\circ)}$

**note:** while putting in mind that the actual voltage of  $V_i = 3e^{j(t+10^\circ)}$  is its real component.

$$V_c = \frac{\sqrt{2}}{2} e^{j(-45^\circ)} V_i$$


$$V_c = \frac{\sqrt{2}}{2} e^{j(-45^\circ)} * (3e^{j(t+10^\circ)})$$

$$V_c = \frac{3\sqrt{2}}{2} e^{j(t-35^\circ)}, \text{ but of course we only care about the real component.}$$

$$V_c = \frac{3\sqrt{2}}{2} \cos(t - 35^\circ)$$

↑  
this result is how imaginary numbers help us.

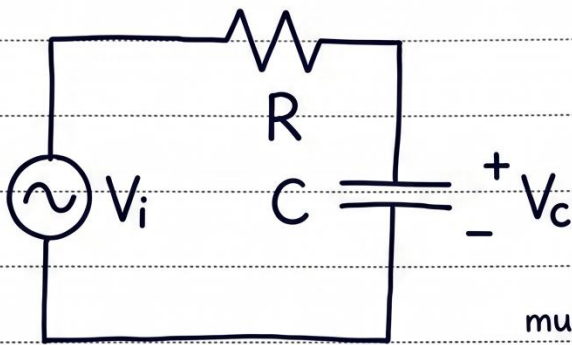And now going back to the original circuit:



using our earlier equation:

$$U_c = \frac{1}{1 + j\omega RC} V_i$$


multiply top and bottom by  $\frac{1}{j\omega C}$ , which is impedance of C.

$$U_c = \frac{1}{1 + j\omega RC} \cdot U_i \times \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_i$$

Notice:

$$U_c = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_i$$

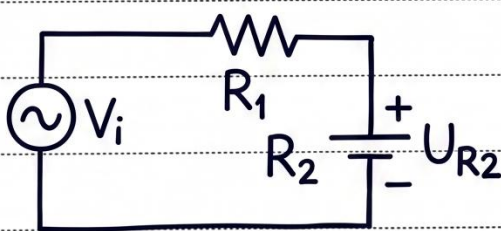that is very similar to the voltage divider equation.



$$U_{R_2} = \frac{R_2}{R_1 + R_2} V_i$$

So, we can treat impedance of Capacitor ( $\frac{1}{j\omega C}$ ) like it is a resistance.  $X_c = \frac{1}{j\omega C}$

so we can apply series and parallel resistance Theorems, voltage and current dividers, but the only difference there will be <sup>imaginary</sup> complex numbers and phase shifts.

Now:

After studying please solve problems on AC circuit analysis and use with it Euler's Formula to let concepts sink in.